

## Lecture 21

### Transmission Lines: RF and Microwave Circuits


---

In this lecture you will learn:

- More about transmission lines
- Impedance transformation in transmission lines
- Transmission line circuits and systems

ECE 303 – Fall 2007 – Farhan Rana – Cornell University

### Transmission Lines: A Review

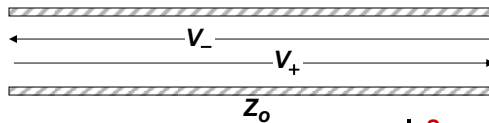

Voltage at any point on the line can be written as:

$$V(z) = V_+ e^{-jkz} + V_- e^{jkz}$$

Current at any point on the line can be written as:

$$I(z) = \frac{V_+}{Z_o} e^{-jkz} - \frac{V_-}{Z_o} e^{jkz}$$


The characteristic impedance of a transmission line is:

$$Z_o = \sqrt{\frac{L}{C}}$$

The dispersion relation for a transmission line is:

$$k = \omega \sqrt{LC}$$

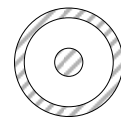Some common examples of transmission lines



Co-axial line




Wire on a ground plane

ECE 303 – Fall 2007 – Farhan Rana – Cornell University
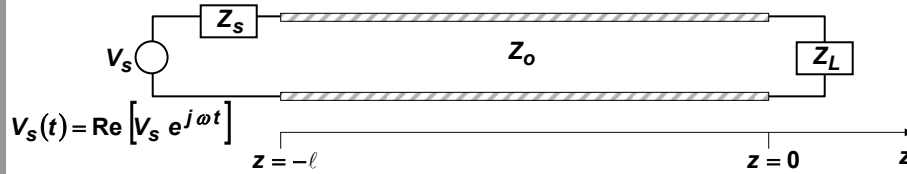
### Transmission Line Circuits

Consider a transmission line connected as shown below:



$Z_0$  = Transmission line impedance  
 $Z_L$  = Load impedance  
 $Z_s$  = Source impedance

In general, voltage on a transmission line is a **superposition** of forward and backward going waves:


$$V(z) = V_+ e^{-jkz} + V_- e^{+jkz}$$

The corresponding current is also a **superposition** of forward and backward going waves:

$$I(z) = \frac{V_+}{Z_0} e^{-jkz} - \frac{V_-}{Z_0} e^{+jkz}$$

ECE 303 – Fall 2007 – Farhan Rana – Cornell University

### Load Boundary Condition

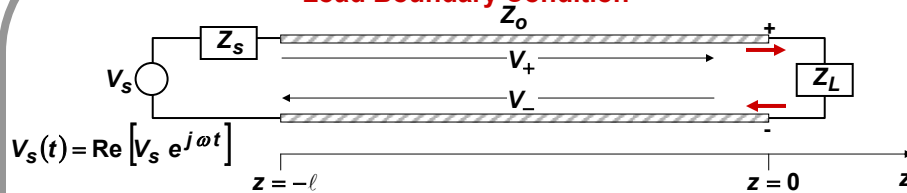

$$V(z) = V_+ e^{-jkz} + V_- e^{+jkz}$$

$$I(z) = \frac{V_+}{Z_0} e^{-jkz} - \frac{V_-}{Z_0} e^{+jkz}$$

**Boundary condition:**

At  $z = 0$  the ratio of the total voltage to the total current must equal the **load impedance**:

$$\frac{V(z=0)}{I(z=0)} = \frac{V_+ + V_-}{V_+/Z_0 - V_-/Z_0} = Z_L$$

$$\Rightarrow \frac{V_-}{V_+} = \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1}$$

This gives us the backward going wave amplitude in terms of the forward going wave amplitude


Define a **load reflection coefficient**  $\Gamma_L$  as:

$$\Gamma_L = \frac{V_-}{V_+} = \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1}$$

ECE 303 – Fall 2007 – Farhan Rana – Cornell University

### Load Reflections


Suppose  $Z_L = 0$  (short):

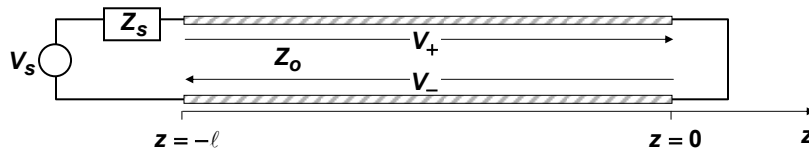

$$\Gamma_L = \frac{V_-}{V_+} = \frac{Z_L/Z_o - 1}{Z_L/Z_o + 1} = -1 \Rightarrow V_- = -V_+$$

$$V(z=0) = V_+ + V_- = 0 \quad \text{and} \quad I(z=0) = \frac{V_+}{Z_o} - \frac{V_-}{Z_o} = 2 \frac{V_+}{Z_o}$$

Suppose  $Z_L = \infty$  (open):

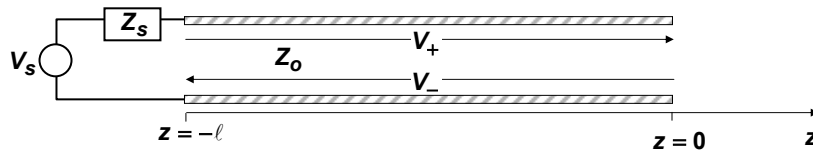


$$\Gamma_L = \frac{V_-}{V_+} = \frac{Z_L/Z_o - 1}{Z_L/Z_o + 1} = +1 \Rightarrow V_- = V_+$$

$$V(z=0) = V_+ + V_- = 2V_+ \quad \text{and} \quad I(z=0) = \frac{V_+}{Z_o} - \frac{V_-}{Z_o} = 0$$

ECE 303 - Fall 2007 - Farhan Rana - Cornell University

### Impedance Transformation - I

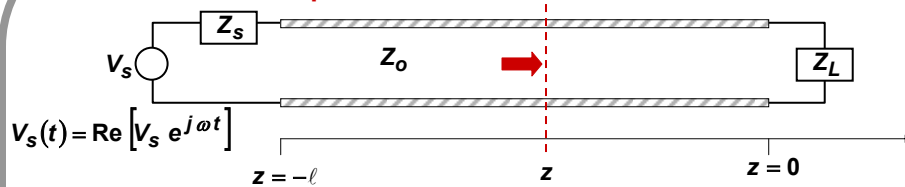

$$V(z) = V_+ (e^{-jkz} + \Gamma_L e^{+jkz}) \quad I(z) = \frac{V_+}{Z_o} (e^{-jkz} - \Gamma_L e^{+jkz})$$

**Question:** What is the impedance  $Z(z)$  looking towards the load at the location  $z$  in the transmission line?


$$Z(z) = \frac{V(z)}{I(z)} = Z_o \frac{1 + \Gamma_L e^{2jkz}}{1 - \Gamma_L e^{2jkz}} \rightarrow \begin{cases} Z(z) = R(z) + jX(z) \\ \text{resistance} \\ \text{reactance} \end{cases}$$

**Check:** What is the impedance  $Z(z=0)$ ?

$$Z(z=0) = Z_o \left. \frac{1 + \Gamma_L e^{2jkz}}{1 - \Gamma_L e^{2jkz}} \right|_{z=0} = Z_o \frac{1 + \Gamma_L}{1 - \Gamma_L} = Z_L \quad \checkmark$$

ECE 303 - Fall 2007 - Farhan Rana - Cornell University

### Impedance Transformation - II

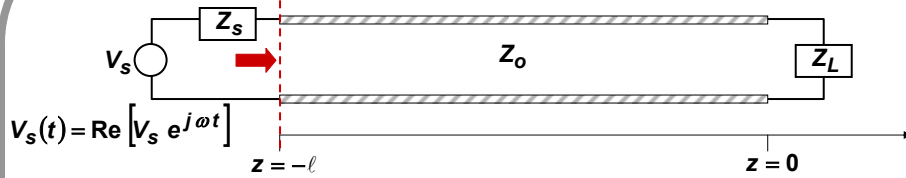


$$V(z) = V_+ (e^{-jkz} + \Gamma_L e^{+jkz}) \quad I(z) = \frac{V_+}{Z_o} (e^{-jkz} - \Gamma_L e^{+jkz})$$

**Question:** What is the impedance  $Z(z=-\ell)$  looking towards the load at the location  $z=-\ell$  in the transmission line



$$Z(z=-\ell) = \frac{V(z=-\ell)}{I(z=-\ell)} = Z_o \frac{1 + \Gamma_L e^{2jkz}}{1 - \Gamma_L e^{2jkz}} \Bigg|_{z=-\ell} = Z_o \frac{1 + \Gamma_L e^{-2jk\ell}}{1 - \Gamma_L e^{-2jk\ell}}$$

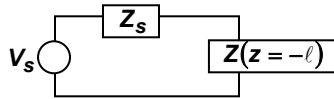Knowing the impedance looking into the line at  $z=-\ell$  we can use the following equivalent circuit:



The load impedance  $Z_L$  has been transformed by the transmission line into the impedance  $Z(z=-\ell)$  at the other end

### Equivalent Circuit

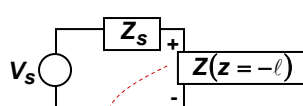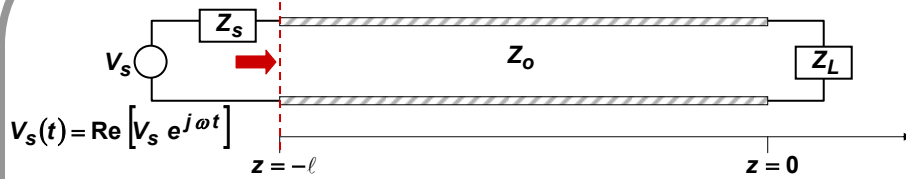

$$\begin{cases} V(z) = V_+ (e^{-jkz} + \Gamma_L e^{+jkz}) \\ I(z) = \frac{V_+}{Z_o} (e^{-jkz} - \Gamma_L e^{+jkz}) \end{cases}$$

The voltage across the impedance  $Z(z=-\ell)$  in the above circuit is:


$$V_s \frac{Z(z=-\ell)}{Z_s + Z(z=-\ell)}$$

So on the transmission line we must have:

$$V(z=-\ell) = V_+ (e^{jk\ell} + \Gamma_L e^{-jk\ell}) = V_s \frac{Z(z=-\ell)}{Z_s + Z(z=-\ell)}$$

$V_+$  can be found from the above equation

### Example – Short Circuit Load - I

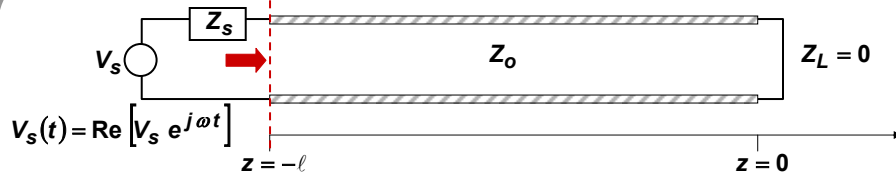

$Z_L = 0$  implies:

$$\Gamma_L = \frac{Z_L/Z_o - 1}{Z_L/Z_o + 1} = -1 \quad \text{and} \quad Z(z = -\ell) = Z_o \frac{1 + \Gamma_L e^{-2jk\ell}}{1 - \Gamma_L e^{-2jk\ell}} = Z_o j \tan(k\ell)$$

Suppose  $k\ell \ll 1$ :


$$\begin{cases} k\ell \ll 1 \Rightarrow \frac{2\pi}{\lambda} \ell \ll 1 \Rightarrow \ell \ll \frac{\lambda}{2\pi} \\ k\ell \ll 1 \Rightarrow \frac{\omega}{v} \ell \ll 1 \Rightarrow \omega \ll \frac{v}{\ell} \end{cases}$$

Then:  $Z(z = -\ell) = Z_o j \tan(k\ell) \approx j Z_o k\ell = j \sqrt{\frac{L}{C}} \omega \sqrt{LC} \ell = j \omega (L\ell)$

- Impedance seen at the source end is **inductive**
- The transmission line appears like one big inductor

ECE 303 – Fall 2007 – Farhan Rana – Cornell University


### Example – Short Circuit Load - II

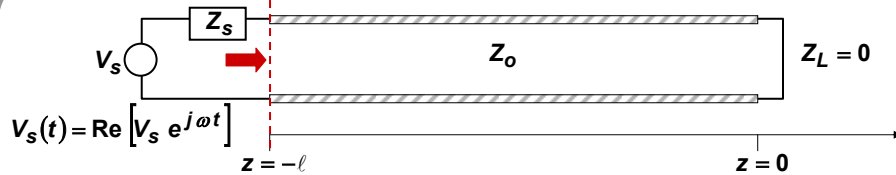

$Z_L = 0$  implies:


$$\Gamma_L = \frac{Z_L/Z_o - 1}{Z_L/Z_o + 1} = -1 \quad \text{and} \quad Z(z = -\ell) = Z_o \frac{1 + \Gamma_L e^{-2jk\ell}}{1 - \Gamma_L e^{-2jk\ell}} = Z_o j \tan(k\ell)$$

$$Z(z = -\ell) = j Z_o \tan(k\ell) = j X$$

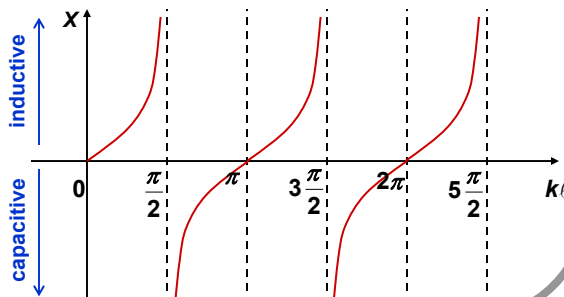

ECE 303 – Fall 2007 – Farhan Rana – Cornell University

### Example – Open Circuit Load - I

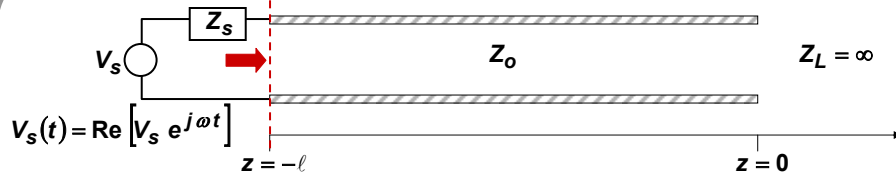

$Z_L = \infty$  implies:

$$\Gamma_L = \frac{Z_L/Z_o - 1}{Z_L/Z_o + 1} = +1 \quad \text{and} \quad Z(z = -l) = Z_o \frac{1 + \Gamma_L e^{-2jk\ell}}{1 - \Gamma_L e^{-2jk\ell}} = -Z_o j \cot(k\ell)$$

Suppose  $k\ell \ll 1$ :


$$\left\{ \begin{array}{l} k\ell \ll 1 \Rightarrow \frac{2\pi}{\lambda} \ell \ll 1 \Rightarrow \ell \ll \frac{\lambda}{2\pi} \\ k\ell \ll 1 \Rightarrow \frac{\omega}{v} \ell \ll 1 \Rightarrow \omega \ll \frac{v}{\ell} \end{array} \right.$$

Then:  $Z(z = -l) = -Z_o j \cot(k\ell) \approx -j \frac{Z_o}{k\ell} = -j \sqrt{\frac{L}{C}} \frac{1}{\omega \sqrt{LC} \ell} = \frac{1}{j\omega(C\ell)}$

- Impedance seen at the source end is **capacitive**
- The transmission line appears like one big capacitor

ECE 303 – Fall 2007 – Farhan Rana – Cornell University


### Example – Open Circuit Load - II

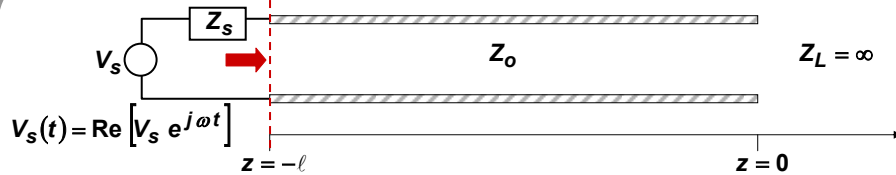

$Z_L = \infty$  implies:


$$\Gamma_L = \frac{Z_L/Z_o - 1}{Z_L/Z_o + 1} = +1 \quad \text{and} \quad Z(z = -l) = Z_o \frac{1 + \Gamma_L e^{-2jk\ell}}{1 - \Gamma_L e^{-2jk\ell}} = -Z_o j \cot(k\ell)$$

$$Z(z = -l) = -j Z_o \cot(k\ell) = jX$$

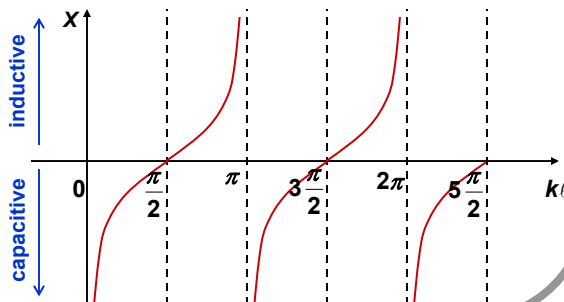

ECE 303 – Fall 2007 – Farhan Rana – Cornell University

### Example – Matched Load

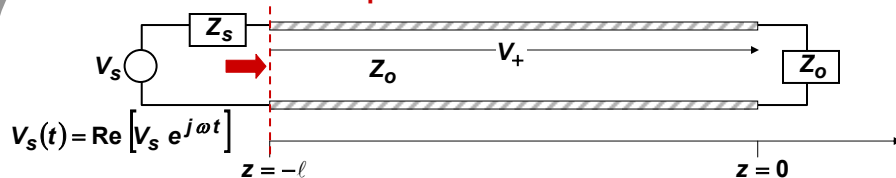

$Z_L = Z_o$  implies:


$$\Gamma_L = \frac{Z_L/Z_o - 1}{Z_L/Z_o + 1} = 0 \quad \text{and} \quad Z(z = -\ell) = Z_o \frac{1 + \Gamma_L e^{-2jk\ell}}{1 - \Gamma_L e^{-2jk\ell}} = Z_o$$

For matched loads:

- The load reflection coefficient  $\Gamma_L$  is zero
- There is no reflected wave generated at the load end (i.e.  $V_- = 0$ )
- The impedance seen at the source end is  $Z_o$  irrespective of the length of the transmission line

ECE 303 – Fall 2007 – Farhan Rana – Cornell University
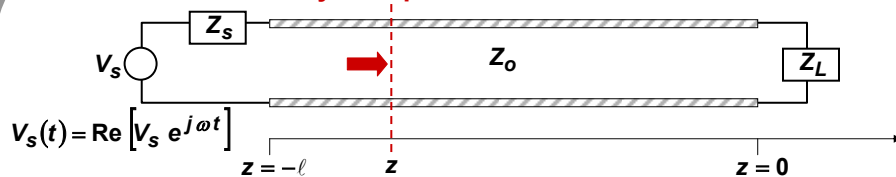
### Periodicity of Impedance Transformation



$$\Gamma_L = \frac{Z_L/Z_o - 1}{Z_L/Z_o + 1} \quad \text{and} \quad Z(z) = Z_o \frac{1 + \Gamma_L e^{2jkz}}{1 - \Gamma_L e^{2jkz}}$$

For locations  $z$  such that  $2kz = 2m\pi$  ( $m$  is an integer) then:

$$Z(z) = Z_o \frac{1 + \Gamma_L e^{2jkz}}{1 - \Gamma_L e^{2jkz}} = Z_o \frac{1 + \Gamma_L}{1 - \Gamma_L} = Z_L \quad \longrightarrow \quad \text{Impedance seen at locations } z = m\pi/k \text{ is also } Z_L$$


Note that:  $2kz = 2m\pi$  but  $k = \frac{2\pi}{\lambda} \Rightarrow z = m \frac{\lambda}{2}$

Impedance seen at locations  $z$  that are integer multiples of half-wavelength from the load end is the load impedance  $Z_L$

More generally:  $Z\left(z \pm m \frac{\lambda}{2}\right) = Z(z)$  Impedance is periodic with period equal to half-wavelength

ECE 303 – Fall 2007 – Farhan Rana – Cornell University

### Standing Wave Ratio

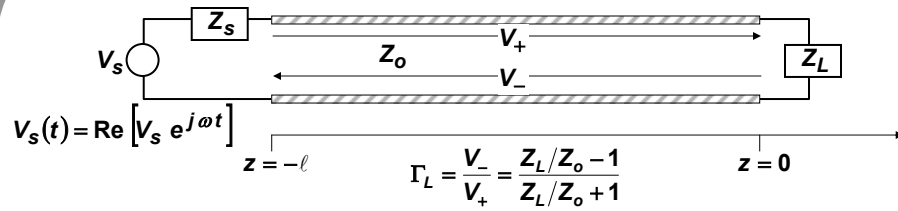

$$V(z) = V_+ e^{-jkz} + V_- e^{jkz} = V_+ (e^{-jkz} + \Gamma_L e^{jkz}) \longrightarrow \left\{ \Gamma_L = |\Gamma_L| e^{j\phi} \right.$$

$$\Rightarrow |V(z)|^2 = |V_+|^2 \left[ 1 + |\Gamma_L|^2 + 2|\Gamma_L| \cos(2kz + \phi) \right]$$

$$\Rightarrow |V(z)| = |V_+| \sqrt{1 + |\Gamma_L|^2 + 2|\Gamma_L| \cos(2kz + \phi)}$$


The interference of forward and backward going waves leads to standing-wave-like behavior

$$\text{Standing Wave Ratio} = \text{SWR} = \frac{|V(z)|_{\max}}{|V(z)|_{\min}} = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$


ECE 303 – Fall 2007 – Farhan Rana – Cornell University
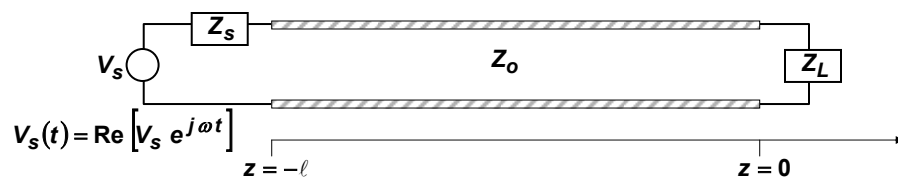
### Thevenin Equivalents of the Source - I


So far we have taken a transmission line circuit:



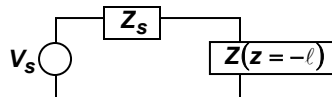And reduced it to the equivalent circuit:



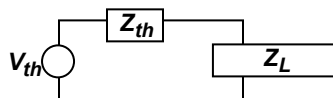Now we want to reduce it to the equivalent circuit:




i.e. we want to produce the Thevenin equivalent of the “source + transmission line” as seen by the load – How do we do that?

ECE 303 – Fall 2007 – Farhan Rana – Cornell University



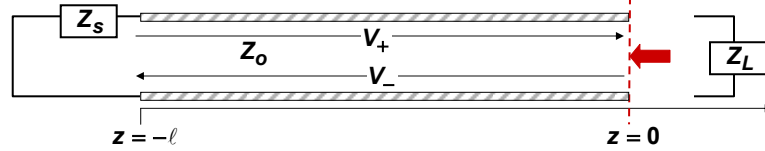
### Thevenin Equivalents of the Source - II

STEP 1: To find  $Z_{th}$  short the voltage source and find the impedance looking in from the load terminals



$$\Gamma_s = \frac{V_+}{V_-} = \frac{Z_s/Z_o - 1}{Z_s/Z_o + 1} \quad \text{and} \quad Z_{th} = Z_o \frac{1 + \Gamma_s e^{-2jk\ell}}{1 - \Gamma_s e^{-2jk\ell}}$$

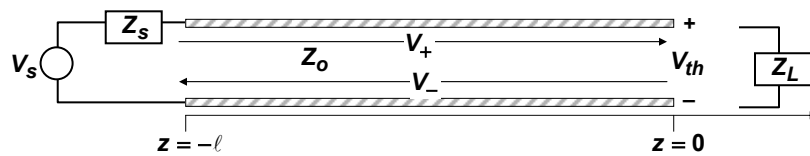
STEP 2: To find  $V_{th}$  remove the load and find the voltage at the load terminals



$$V_{th} = 2V_+ = \frac{V_s}{\cos(k\ell)} \frac{-jZ_o \cot(k\ell)}{Z_s - jZ_o \cot(k\ell)}$$

ECE 303 – Fall 2007 – Farhan Rana – Cornell University
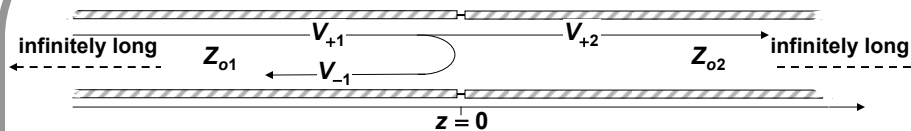
### Unmatched Infinite Transmission Lines



Consider the situation above where we have two unmatched transmission lines connected together

$$\begin{aligned} V_1(z) &= V_{+1} e^{-jk_1 z} + V_{-1} e^{+jk_1 z} & V_2(z) &= V_{+2} e^{-jk_2 z} \\ I_1(z) &= \frac{V_{+1}}{Z_{o1}} e^{-jk_1 z} - \frac{V_{-1}}{Z_{o1}} e^{+jk_1 z} & I_2(z) &= \frac{V_{+2}}{Z_{o2}} e^{-jk_2 z} \end{aligned}$$

Boundary Conditions

- (1) At  $z=0$  the voltage on both the transmission lines must be the same
- (2) At  $z=0$  the current on both the transmission lines must be the same

$$(1) \Rightarrow V_{+1} + V_{-1} = V_{+2} \quad \text{and} \quad (2) \Rightarrow \frac{V_{+1}}{Z_{o1}} - \frac{V_{-1}}{Z_{o1}} = \frac{V_{+2}}{Z_{o2}}$$


$$\Gamma = \frac{V_{-1}}{V_{+1}} = \frac{Z_{o2}/Z_{o1} - 1}{Z_{o2}/Z_{o1} + 1}$$

$$T = \frac{V_{+2}}{V_{+1}} = \frac{2Z_{o2}/Z_{o1}}{Z_{o2}/Z_{o1} + 1}$$

How does one avoid reflections at the junction of the two transmission lines?

ECE 303 – Fall 2007 – Farhan Rana – Cornell University
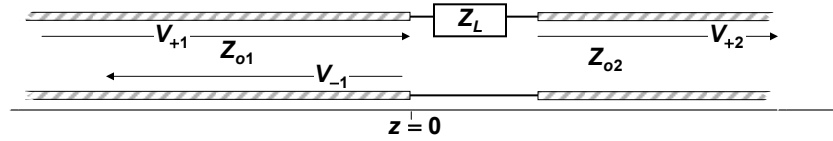
### Power Splitting in Microwave Circuits




Input wave:  $V_i(z) = V_{+1} e^{-jk_1 z}$

Transmitted wave:  $V_t(z) = V_{+2} e^{-jk_2 z}$

Reflected wave:  $V_r(z) = V_{-1} e^{+jk_1 z}$

**Goal:** Need to find  $V_{+2}$  and  $V_{-1}$  in terms of  $V_{+1}$

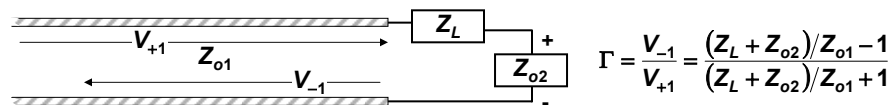**STEP 1:** Cast the circuit in the following equivalent form and find  $V_{-1}$



**STEP 2:** Voltage  $V_{+2}$  is the same as the voltage across the impedance  $Z_{o2}$  in the equivalent circuit

$$V_{+2} = [V_i(z=0) + V_r(z=0)] \frac{Z_{o2}}{Z_L + Z_{o2}} = V_{+1} (1 + \Gamma) \frac{Z_{o2}}{Z_L + Z_{o2}}$$